


~~COMPONENTS IN SERIES GET THE SAME CURRENT~~

COMPONENTS IN SERIES GET
 \triangle THE SAME CURRENT (don't add unnecessary currents)

Steps:

1. Assign currents to branches (i_1, i_2, i_3)

2. Assign polarity to resistances

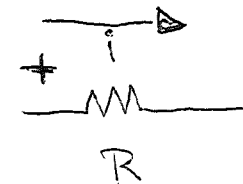

3. Write Kirchhoff laws

4. Solve system of equations (" n " equations for " n " variables)

Ex. 3.2


PAGE 1

$$U_1 = U_2 = U_3 = 10 \text{ V}$$

$$R_1 = R_2 = R_3 = 2 \Omega$$

$$R_4 = 50 \Omega$$

$$R_5 = 100 \Omega$$

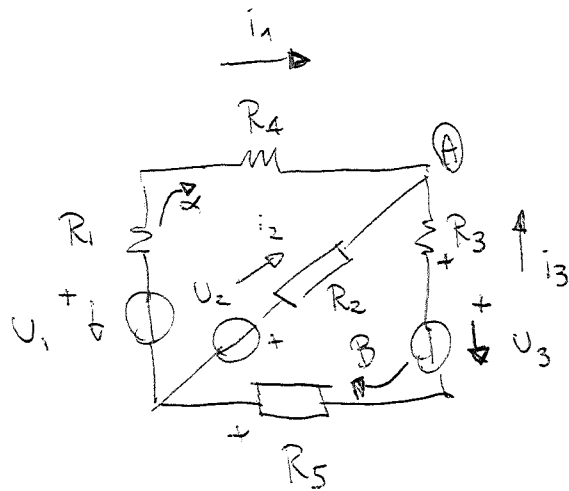

$$\textcircled{A} \quad i_1 + i_2 + i_3 = 0$$

$$\textcircled{A}' \quad i_3 = -(i_1 + i_2)$$

$$\textcircled{A} : -U_1 + i_1 R_1 + i_1 R_4 - i_2 R_2 + U_2 = 0$$

$$\textcircled{B} : -i_3 R_3 + U_3 - i_3 R_5 - U_2 + i_2 R_2 = 0$$

$$\textcircled{A}' \text{ into } \textcircled{B} : (i_1 + i_2) R_3 + U_3 + (i_1 + i_2) R_5 - U_2 + i_2 R_2 = 0$$

$$i_1 (R_3 + R_5) + i_2 (R_3 + R_5 + R_2) + U_3 - U_2 = 0$$

$$\textcircled{B}' : \quad \text{[scribbled out]} \quad i_2 = \frac{U_2 - U_3 - i_1 (R_3 + R_5)}{R_3 + R_5 + R_2}$$

ⓑ' into ⓐ :

$$-U_1 + i_1 R_1 + i_1 R_4 + U_2 - \frac{R_2}{R_3 + R_5 + R_2} \left(U_2 - U_3 - i_1 (R_3 + R_5) \right) = 0$$

$$-U_1 + i_1 R_1 + i_1 R_4 + U_2 - \frac{1}{R_T} \left(U_2 - U_3 - i_1 (R_3 + R_5) \right) = 0$$

$$-U_1 R_T + i_1 R_1 R_T + i_1 R_4 R_T + U_2 R_T - U_2 + U_3 + i_1 (R_3 + R_5) = 0$$

$$i_1 (R_1 R_T + R_4 R_T + R_3 + R_5) = U_1 R_T - U_2 R_T + U_2 - U_3$$

$$i_1 = \frac{U_1 R_T - U_2 R_T + U_2 - U_3}{R_1 R_T + R_4 R_T + R_3 + R_5} = \frac{0 + 0}{-} = 0 \quad \boxed{i_1}$$

$\boxed{i_1}$ into ⓑ' : $i_2 = \frac{0 - 0}{-} = 0$. $\boxed{i_1}$ and $\boxed{i_2}$ into ⓐ : $i_3 = -0$.

Ex 3.2 VARIATION

PAGE 3

Consider 3.2 but with $V_3 = 15 \text{ V}$.

$$\boxed{i_1} \quad i_1 = \frac{V_1 R_T - V_2 R_T + V_2 - V_3}{R_1 R_T + R_4 R_T + R_3 + R_5} = \frac{0 + 10 - 15}{R_T(R_1 + R_4) + R_3 + R_5} = -\frac{5}{52.52 + 2 + 100} = -\frac{5}{2806} =$$

$$= i_1 = -1.7 \text{ mA}.$$

$\boxed{i_1}$ into $\textcircled{\text{B}}$:

$$i_2 = \frac{V_2 - V_3 + 1.7 \text{ mA} (R_3 + R_5)}{R_3 + R_5 + R_2} = \frac{-5 + 1.7 \text{ mA} \cdot 102 \Omega}{104 \Omega} = -0.0464 \text{ A}.$$

$$\boxed{i_1} \text{ and } \boxed{i_2} \text{ into A: } i_3 = -(i_1 + i_2) = -(-1.8 \text{ mA} - 0.0464 \text{ A}) = 0.0482 \text{ A}.$$

Ex. 3.2
MATRIX WAY

PAGE 4

$$\textcircled{A} \quad i_1 + i_2 + i_3 = 0$$

$$\textcircled{B} \quad i_1(R_1 + R_4) - i_2 R_2 = V_1 - V_2$$

$$\textcircled{C} \quad i_2 R_2 + i_3(-R_3 - R_5) = V_2 - V_3$$

$$\begin{bmatrix} 1 & 1 & 1 \\ R_1 + R_4 & -R_2 & 0 \\ 0 & R_2 & -R_3 - R_5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ V_1 - V_2 \\ V_2 - V_3 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 & 1 \\ 52 & -2 & 0 \\ 0 & 2 & -102 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = A^{-1} \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$